


This exam includes five problems. Note that the last one is at the other side of the paper. Each problem gives 10 points at maximum.

1.

Answer shortly, with a few words, to the following questions.

- a) Name the following symbols related to feedback: A_F , A , β , and $A\beta$.
- b) You need to know the frequency limit of a transistor biased as an amplifier. Which transistor model do you use? Draw the model.
- c) How can you recognize an active circuit from its scattering parameters?
- d) When analyzing digital systems, what does multiplying by z^{-1} mean?


2.

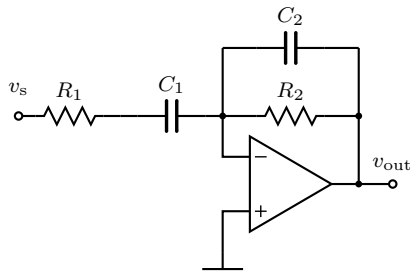

An acoustic sensor is represented by v_s in the figure. The band-pass filter in the figure is specified to pass an input signal with its specified bandwidth. Determine the bandwidth and center frequency of the circuit when the op-amp is assumed ideal.

Hint: Determine first the transfer function $\frac{v_{out}}{v_s}$.

3.

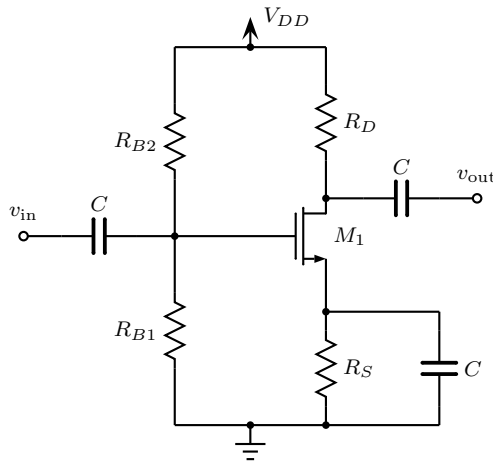

The operating point of the transistor is $V_{GS} = 3\text{ V}$, $V_{DS} = 10\text{ V}$ and $I_D = 4\text{ mA}$.


- a) Calculate the open-circuit voltage gain for the CS-amplifier.
- b) Calculate the input impedance and the output impedance of the CS-amplifier.

You can neglect the channel-length modulation in this exercise. Capacitances C are large at the frequency of the input signal.

Hint: Start by drawing the small signal model.

$$\begin{aligned} R_{B1} &= 10\text{ k}\Omega & R_{B2} &= 30\text{ k}\Omega & R_D &= 2\text{ k}\Omega \\ R_S &= 500\ \Omega & V_{DD} &= 20\text{ V} & k'_n \frac{W}{L} &= 2\text{ mA/V}^2 \\ V_t &= 1\text{ V}. \end{aligned}$$

4.

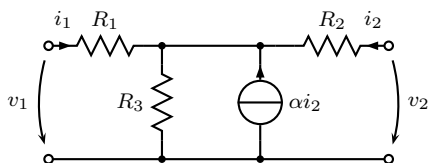

An electronic amplifier has the circuit shown in the figure. Determine the impedance parameters for the circuit.

$$\begin{aligned} z_{11} &= \left. \frac{v_1}{i_1} \right|_{i_2=0} & z_{12} &= \left. \frac{v_1}{i_2} \right|_{i_1=0} \\ z_{21} &= \left. \frac{v_2}{i_1} \right|_{i_2=0} & z_{22} &= \left. \frac{v_2}{i_2} \right|_{i_1=0} \end{aligned}$$


5.

Answer this question by writing and drawing on this paper and returning it.


- a) Name the type of filter for each of the figures.
- b) Mark f_0 , f_L and f_H on the figure(s) (where applicable!).
- c) What are the locations of poles and zeros in each case?

Note: all filters are of the second-order!


Filter type is: _____

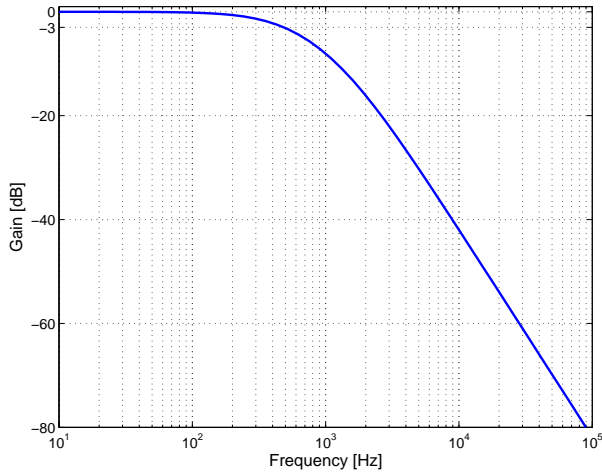


Filter type is: _____

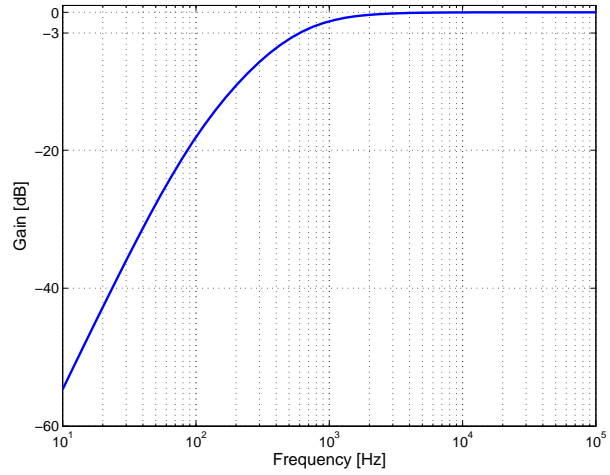

Filter type is: _____

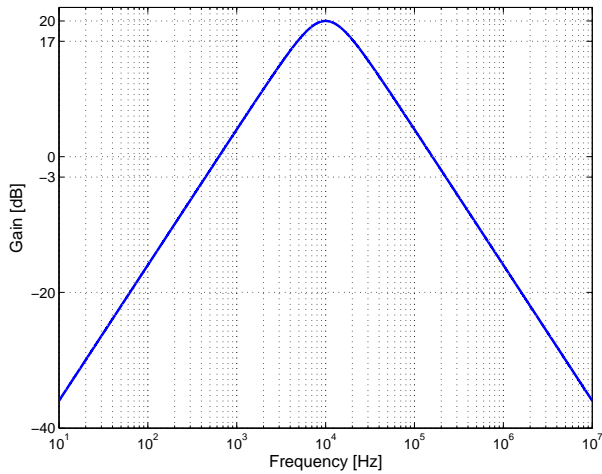

Filter type is: _____

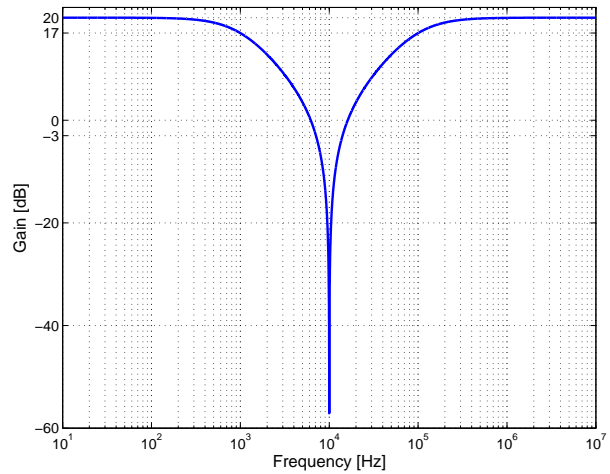

Name: _____

Student number: _____

0.1


Answer shortly, with a few words, to the following questions.

- Name the following symbols related to feedback: A_F , A , β , and $A\beta$.
 - You need to know the frequency limit of a transistor biased as an amplifier. Which transistor model do you use? Draw the model.
 - How can you recognize an active circuit from its scattering parameters?
 - When analyzing digital systems, what does multiplying by z^{-1} mean?
-

a)

- A_F : $A_F = \frac{A}{1+A\beta}$, closed loop gain
- A : Open loop gain
- β : Feedback
- $A\beta$: Loop Gain

b)

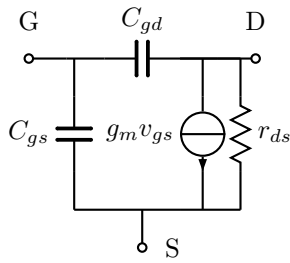


$$\begin{aligned}
 g_m &= \sqrt{2I_D k'_n \frac{W}{L}} \\
 &= k'_n \frac{W}{L} (V_{GS} - V_{tn}) \\
 r_{ds} &\approx \frac{1}{\lambda I_D}
 \end{aligned}$$

c) If the magnitude of any S parameter is larger than 1 or


$$|S_{11}|^2 + |S_{21}|^2 > 1$$

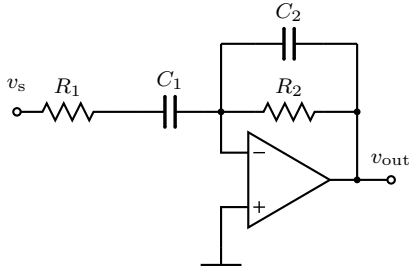d) Multiplying by z^{-1} models a delay of one time period of sampling frequency.



An acoustic sensor is represented by v_s in the figure. The band-pass filter in the figure is specified to pass an input signal with its specified bandwidth. Determine the bandwidth and center frequency of the circuit when the op-amp is assumed ideal.

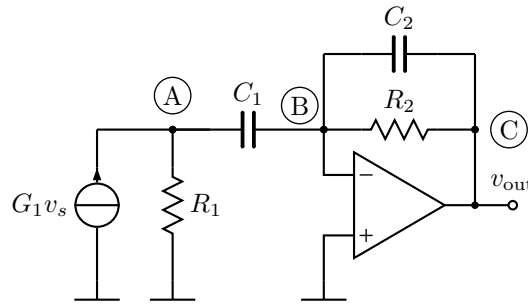Hint: Determine first the transfer function $\frac{v_{out}}{v_s}$.



$$\begin{bmatrix} G_1 + sC_1 & -sC_1 & 0 \\ -sC_1 & G_2 + sC_1 + sC_2 & -G_2 - sC_2 \\ 0 & -G_2 - sC_2 & G_2 + sC_2 \end{bmatrix} \begin{bmatrix} U_A \\ U_B \\ U_C \end{bmatrix} = \begin{bmatrix} G_1 v_s \\ 0 \\ I_{out} \end{bmatrix}$$


Same voltage in input nodes of opamp. Node B is at the ground potential and the corresponding column can be removed.

$$\begin{bmatrix} G_1 + sC_1 & 0 \\ -sC_1 & -G_2 - sC_2 \end{bmatrix} \begin{bmatrix} U_A \\ U_C \end{bmatrix} = \begin{bmatrix} G_1 v_s \\ 0 \end{bmatrix}$$

$$H(s) = \frac{v_{out}}{v_s} = -\frac{-sC_1 G_1}{(G_1 + sC_1)(G_2 + sC_2)} = \frac{sC_1 G_1}{s^2 C_1 C_2 + s(C_1 G_2 + C_2 G_1) + G_1 G_2} = \frac{h(s)}{s^2 + s\frac{\omega_0}{Q} + \omega_0^2}$$

$$\omega_0 = \sqrt{\frac{G_1 G_2}{C_1 C_2}}$$
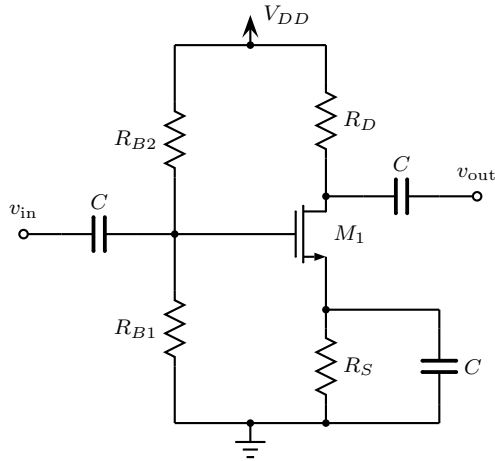
$$\Delta\omega = \frac{\omega_0}{Q} = \frac{C_1 G_2 + C_2 G_1}{C_1 C_2}$$



The operating point of the transistor is $V_{GS} = 3\text{ V}$, $V_{DS} = 10\text{ V}$ and $I_D = 4\text{ mA}$.

a) Calculate the open-circuit voltage gain for the CS-amplifier.


b) Calculate the input impedance and the output impedance of the CS-amplifier.

You can neglect the channel-length modulation in this exercise. Capacitances C are large at the frequency of the input signal.

Hint: Start by drawing the small signal model.

$$\begin{aligned} R_{B1} &= 10\text{ k}\Omega & R_{B2} &= 30\text{ k}\Omega & R_D &= 2\text{ k}\Omega \\ R_S &= 500\ \Omega & V_{DD} &= 20\text{ V} & k'_n \frac{W}{L} &= 2\text{ mA/V}^2 \\ V_t &= 1\text{ V}. \end{aligned}$$

a) Small signal:

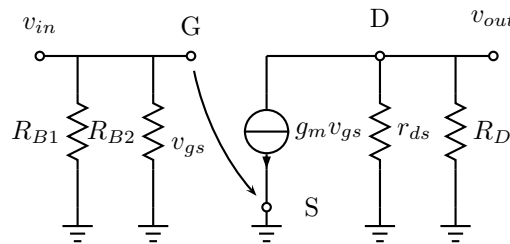

Now we can calculate the parameters with the DC-operation point values:

$$\begin{aligned} g_m &= \sqrt{2I_D k'_n \frac{W}{L}} = k'_n \frac{W}{L} (V_{GS} - V_{tn}) = 4\text{ mS} \\ r_{ds} &\approx \frac{1}{\lambda I_D} \approx \infty, \end{aligned}$$

because we were told to ignore the channel length modulation, so that means there is no resistor r_{ds} in our circuit.

Next, we will calculate the open circuit voltage (as we have no load, the output of the open circuit will just be the same as v_{out} in our figure):

$$v_{out} = -g_m R_D v_{gs} = -g_m R_D (v_g - v_s) = -g_m R_D (v_{in} - 0) = -g_m R_D v_{in} \quad (1)$$


$$A_{vo} = \frac{v_{out,open}}{v_{in}} = -g_m R_D = -8 \quad (2)$$

b) Using the figure from a-part, we get

$$R_{in} = R_{B1} || R_{B2} = 7.5\text{ k}\Omega \quad (3)$$

$$R_{out} = R_D = 5\text{ k}\Omega \quad (4)$$

0.4

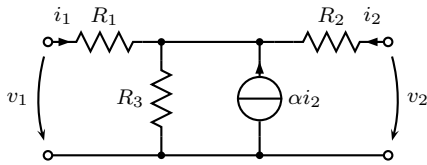


An electronic amplifier has the circuit shown in the figure. Determine the impedance parameters for the circuit.

$$z_{11} = \left. \frac{v_1}{i_1} \right|_{i_2=0} \quad z_{12} = \left. \frac{v_1}{i_2} \right|_{i_1=0}$$

$$z_{21} = \left. \frac{v_2}{i_1} \right|_{i_2=0} \quad z_{22} = \left. \frac{v_2}{i_2} \right|_{i_1=0}$$


Assume first, $i_2 = 0$:

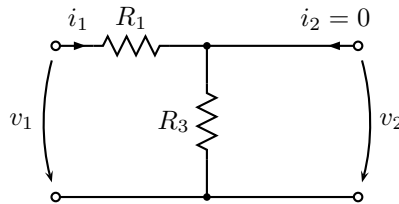

$$z_{11} = \left. \frac{v_1}{i_1} \right|_{i_2=0} = R_1 + R_3$$

$$z_{21} = \left. \frac{v_2}{i_1} \right|_{i_2=0} = R_3$$

Assume next, $i_1 = 0$:

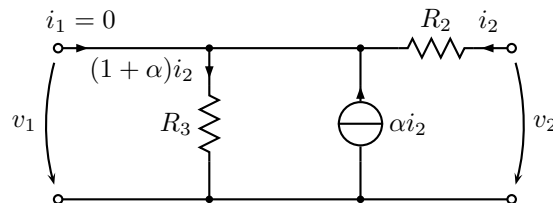

Applying the Kirchhoff's current law, the current through the resistor R_3 is $(1 + \alpha)i_2$.

$$z_{12} = \left. \frac{v_1}{i_2} \right|_{i_1=0} = (1 + \alpha)R_3$$

$$z_{22} = \left. \frac{v_2}{i_2} \right|_{i_1=0} = R_2 + (1 + \alpha)R_3$$


0.5

Answer this question by writing and drawing on this paper and returning it.


- Name the type of filter for each of the figures.
- Mark f_0 , f_L and f_H on the figure(s) (where applicable!).
- What are the locations of poles and zeros in each case?

Note: all filters are of the second-order!


Filter type is: _____

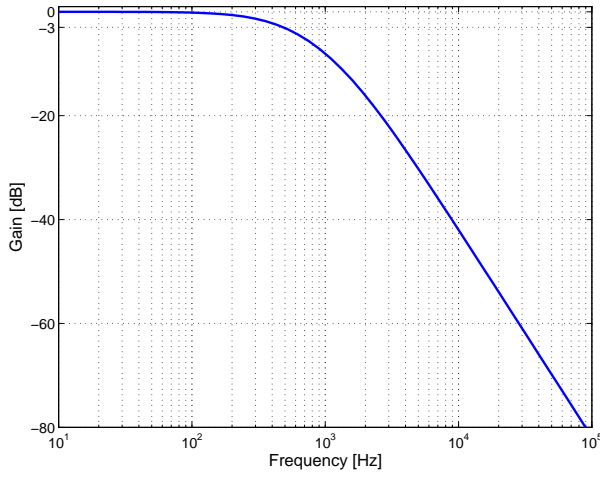


Filter type is: _____

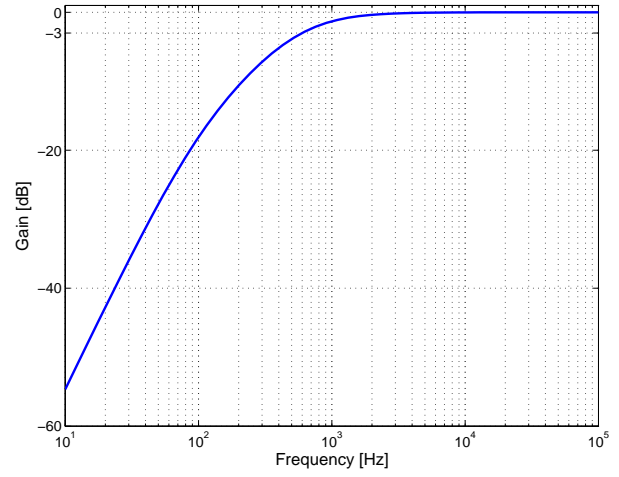

Filter type is: _____

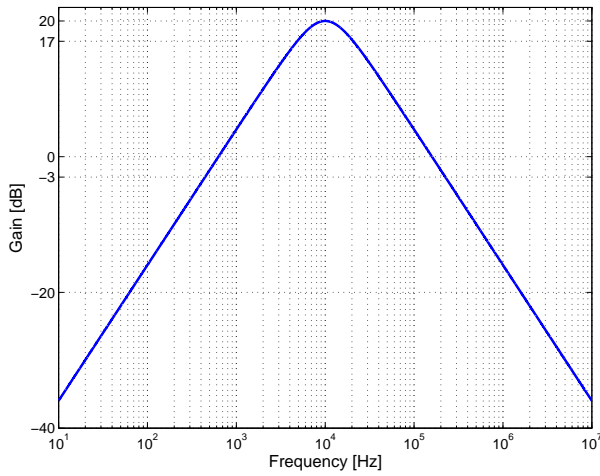

Filter type is: _____

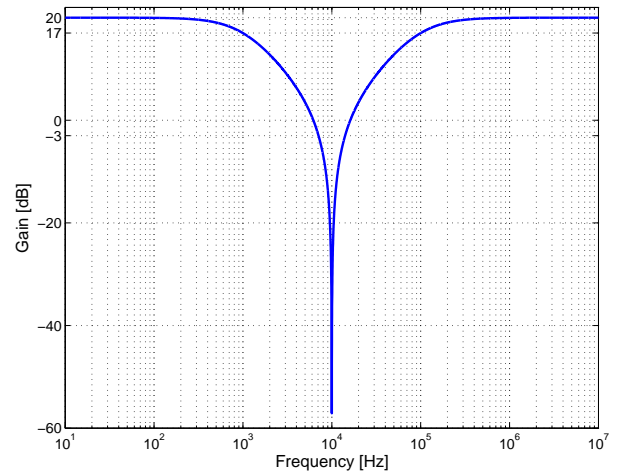


Name: _____

Student number: _____

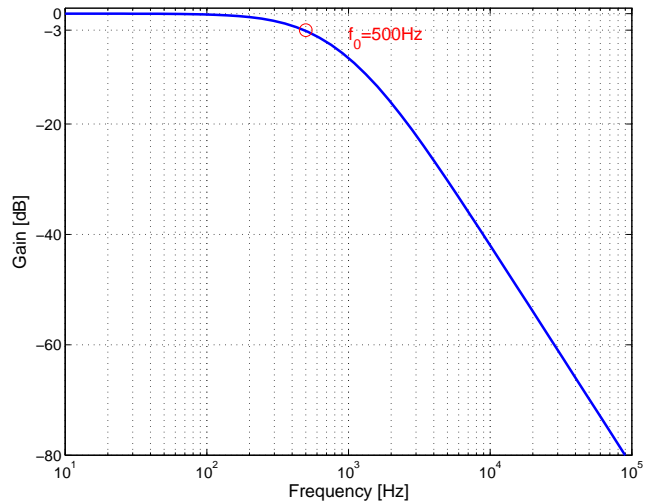
a) Low-pass filter.

Two poles at $f_0 = 500\text{Hz}$ (two zeroes at ∞).



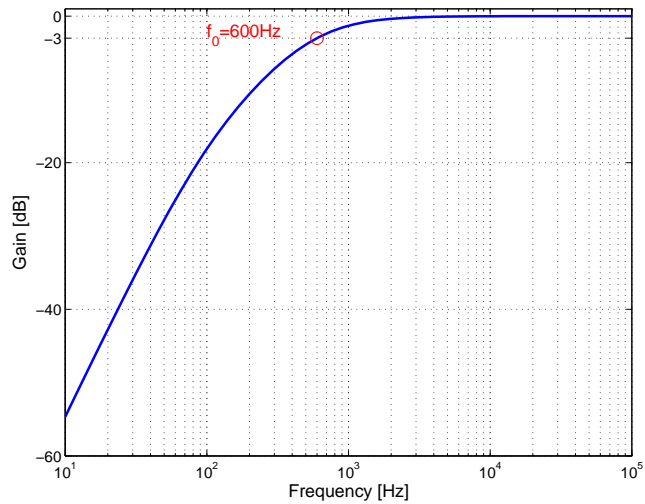
b) High-pass filter.

Two zeroes at 0 and two poles at $f_0 = 600\text{Hz}$.



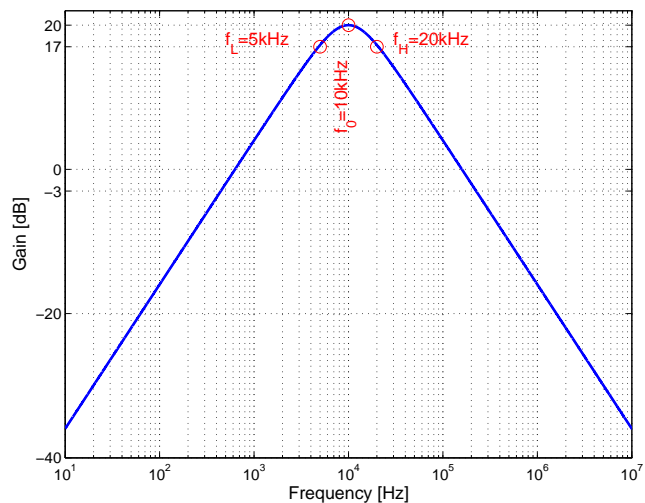c) Band-pass filter.

One zero at 0, two poles at $f_0 = 10\text{kHz}$ (one zero at ∞).



d) Band-stop filter.

One pole at $f_L = 1\text{kHz}$, two zeroes at $f_0 = 10\text{kHz}$ and one pole at $f_H = 100\text{kHz}$.

