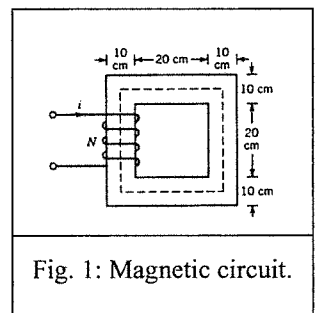


1. Explain the following concepts, use drawings and equations when adequate.
 - a) Describe the construction and operation of a separately excited DC-motor. (hint: stator, rotor, commutator, and operation principles) (2 p.)
 - b) Explain the effect of an external resistance connected to the rotor of a wound-rotor induction motor on its speed-torque profile. (hint: slip-torque plot at different resistances) (2 p.)
 - c) Explain how the rotating field is produced in the air gap of an AC machine (hint: 3-phases winding in the stator, mmf 's of each phase and their sum) (2 p.)
 - d) Explain the static stability limits of a synchronous machine. What are these limits? Why they are important? What happens if any of them exceeds? (hint: use drawing in the PQ plan) (2p.)
 - e) Draw the complete single-phase equivalent circuit of a transformer and explain what each of its component represents physically (2p.)
 - f) Explain how the power factor of a synchronous machine can be controlled, while the machine is delivering a constant active power. Draw the phasor diagram of the machine at unity power factor and lagging power factor (hint: use the terminal voltage as reference, 0 deg, and arbitrary currents with different angles) (2p.)

2. The magnetic circuit of Fig. 1 has a core of relative permeability $\mu_r = 2000$. The depth of the core is 5 cm. The coil has 400 turns and carries a current of 1,5 A. The dashed line shows the average flux path.
 - a) Draw the magnetic equivalent circuit and calculate its parameters (mmf and reluctances) (2 p.)
 - b) Calculate the flux and the flux density in the core from the equivalent circuit (2 p.)
 - c) Determine the inductance of the coil from the results of (b) (2 p.)




3. A three phases, 250 kW, 460 V, 60 Hz, eight-poles, star-connected induction machine is connected to a 460 V infinite bus and is running as a generator at a slip $s = -2,5\%$. The IEEE-recommended equivalent circuit of the machine in Fig. 2 has the following parameters:

$$R_1 = 0,015\Omega; \quad R_2' = 0,035\Omega;$$

$$X_1 = 0,145\Omega; \quad X_2' = 0,145\Omega; \quad X_m = 6,5\Omega$$

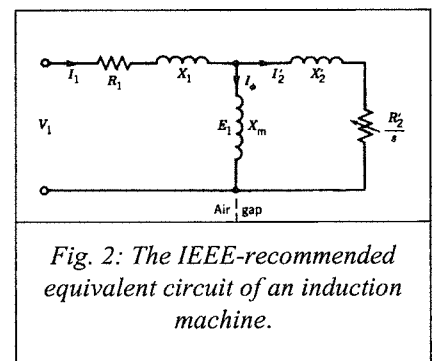- a) Determine the speed of the rotor (2 p.)
- b) Determine the power delivered to the infinite bus and the power factor (2 p.)
- c) Determine the efficiency of the generator. The rotational and core losses are 3 kW (2 p.)



4. A 1 MVA, 3 phases, 2300 V, 60 Hz, 10 poles, star-connected cylindrical-rotor synchronous motor is connected to an infinite bus. The synchronous reactance is 4,23 Ω . The synchronous motor delivers 746 kW and operates at 0,85 power factor leading. All losses may be neglected.
 - a) Determine the armature current I_a (2p)
 - b) Determine the excitation voltage E_f and the load angle δ . (2 p.)
 - c) Determine the maximum power the motor can deliver for the excitation of part (a). (2 p.)

Evaluation:

Grade	Lower limit	Upper limit
0	0	13
1	14	16
2	17	19
3	20	22
4	23	26
5	27	30

Some useful formulas and drawings:

Magnetic reluctance: $\mathfrak{R} = \frac{l}{\mu A}$


Magnetomotive force: $F = Ni$

Force pressure: $F_m = \frac{B_g^2}{2\mu_0}$

Speed of AC-machine: $n = \frac{120f}{p}$ (p is the number of poles!)

Slip of induction machine: $s = \frac{n_s - n}{n_s}$

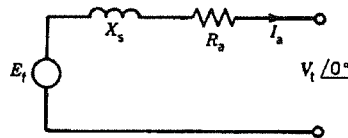Equivalent circuit of a synchronous generator:



Real power of a synchronous machine: $P_{3\phi} = \frac{3|V_t||E_f|}{|X_s|} \sin \delta = P_{\max} \sin \delta$

Imaginary/Reactive power of a synchronous machine: $Q_{3\phi} = \frac{3|V_t||E_f|}{|X_s|} \cos \delta - \frac{3|V_t|^2}{|X_s|}$

Convention: lagging reactive power positive -- > phase angle of current negative

AC active power: $P = 3V_{ph}I_{ph} \cos \phi = \sqrt{3}VI \cos \phi$

Magnetic permeability: $\mu = \mu_r \mu_0$; $\mu_0 = 4\pi 10^{-7} \text{ Hm}^{-1}$

In ac systems, the electrical quantities are complex-valued; they have real and imaginary parts (or amplitude and phase angle)

For an asynchronous machine, we can write the rotor resistance part as: $\frac{R_2'}{s} = R_2' + \frac{(1-s)R_2'}{s}$