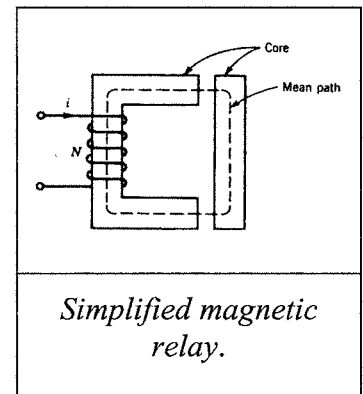



1. Explain the following concepts, use drawings and equations when adequate.
  - a) Describe the stator and rotor constructions and the principle of operation of a **separately excited DC-machine**. (Hint: field and armature, forces on conductors and torque, induced voltage, commutator and brushes, etc...) (3p.)
  - b) Explain the three running modes of operation of an induction machine by drawing the Torque-Speed (or Slip) curve and give the range of the slip for each mode of operation (3 p.)
  - c) Draw the complete single-phase equivalent circuit of a transformer and explain what each of its component represents (3 p.)
  - d) Explain the static stability limits of a synchronous machine. What are these limits? Why they are important? What happens if any of them exceeds? (hint: use drawing in the PQ plan) (3 p.)

2. The magnetic relay in the figure has a coil of 500 turns carrying a current  $I_{dc} = 4,19$  A. The mean core path length is  $l_c = 360$  mm and the air gap is  $l_g = 1,5$  mm. The relative permeability of the core is  $\mu_c = 1250$  and its cross-section is  $A_c = 100$  mm<sup>2</sup>. Neglect flux fringing in the air gaps.



- a) Draw the equivalent magnetic circuit of the relay and calculate its parameters, (MMF and reluctances) (2 p.)
- b) Calculate the flux density in the air gap (use the circuit in (a)) (2 p.)
- c) Calculate the total force acting on the moving part (2 p.)

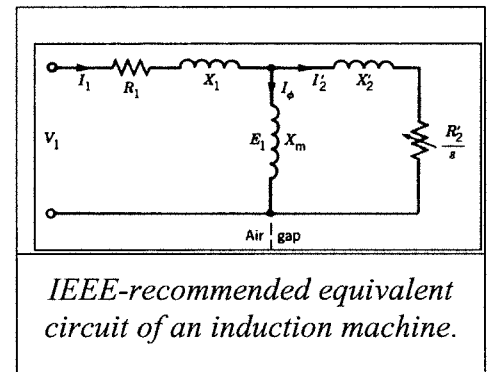3. A three phases, 250 kW, 460 V, 60 Hz, eight poles, star-connected induction machine is connected to a 460 V infinite bus and is running as a generator at a slip  $s = -2,5$  %. The equivalent circuit of the machine, in the figure, has the following parameters



$$R_1 = 0,015\Omega; \quad R_2' = 0,035\Omega;$$

$$X_1 = 0,145\Omega; \quad X_2' = 0,145\Omega; \quad X_m = 6,5\Omega$$

- a) Determine the speed of the rotor (2 p.)
  - b) Determine the power delivered to the infinite bus and the power factor (2 p.)
  - c) Determine the efficiency of the generator. The rotational and core losses are 3 kW (2 p.)
4. A 2-pole DC-motor connected to 345 V supply draws 39 A current and produces 11 kW mechanical power at 1500 rpm.
    - a) Calculate the mechanical torque and resistive losses in armature winding ( $R_a=0,8706$   $\Omega$ ) (2 p.)
    - b) Calculate the input power of the motor and its efficiency (neglect field winding losses) (2 p.)
    - c) Calculate the back electromotive force  $E_a$  when the flux factor at nominal field current is  $k_\phi=1,895$  Vs/rad (2 p.)

Evaluation:

Grade	Lower limit	Upper limit
0	0	13
1	14	16
2	17	19
3	20	22
4	23	26
5	27	30

Some useful formulas and drawings:

Magnetic reluctance:  $\mathfrak{R} = \frac{l}{\mu A}$


Magnetomotive force:  $F = Ni$

Force pressure:  $F_m = \frac{B_g^2}{2\mu_0}$

Speed of AC-machine:  $n = \frac{120f}{p}$  ( $p$  is the number of poles!)

Slip of induction machine:  $s = \frac{n_s - n}{n_s}$

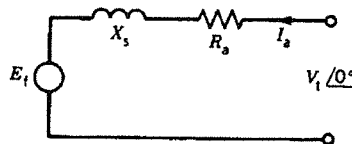Equivalent circuit of a synchronous motor:



Convention: lagging reactive power positive -- > phase angle of current negative

AC active power:  $P = 3V_{ph}I_{ph} \cos \phi = \sqrt{3}VI \cos \phi$

Magnetic permeability:  $\mu = \mu_r \mu_0; \quad \mu_0 = 4\pi 10^{-7} \text{ Hm}^{-1}$