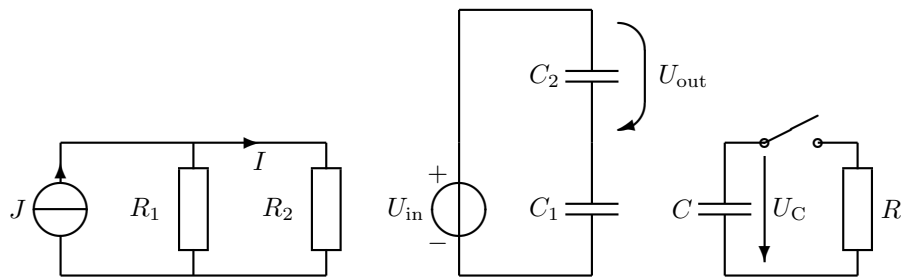


Answer all four questions!




**Assignment 1**

Find the current  $I$  (3 points), the transfer function  $F(s) = \frac{U_{out}}{U_{in}}$  (3 points) and the voltage  $U_C(t)$ , when the switch is closed at time  $t = 0$  (4 points). The component values are

$$J = 1 \text{ mA} \quad R_1 = 3 \text{ k}\Omega \quad R_2 = 6 \text{ k}\Omega \quad C_1 = C_2 = 10 \text{ nF} \quad C = 100 \mu\text{F} \quad R = 100 \text{ k}\Omega$$

and the initial voltage of the capacitor  $C$  is  $U_C(0) = 10 \text{ V}$ .

**Assignment 2**

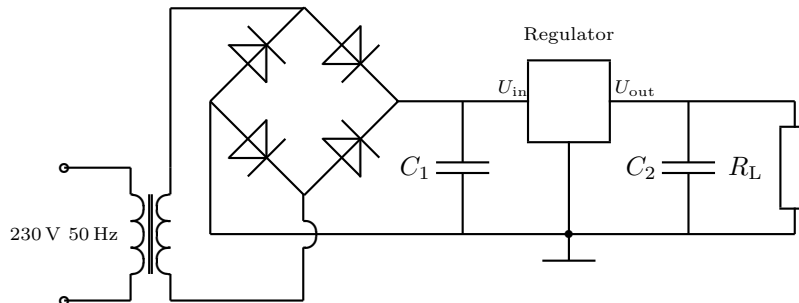


The input voltage of the regulator can vary between  $8 \text{ V} \dots 15 \text{ V}$ . The current taken by the load and the regulator is  $500 \text{ mA}$ . Calculate the value for the capacitor  $C_1$  (5 points) and the maximum reverse voltage for diodes  $U_{reverse}$  (3 points). Calculate also the rms value for the output voltage of the transformer (2 points).


Bonus question (2 points): find the maximum current through the diodes in the rectifier bridge.

**Assignment 3**

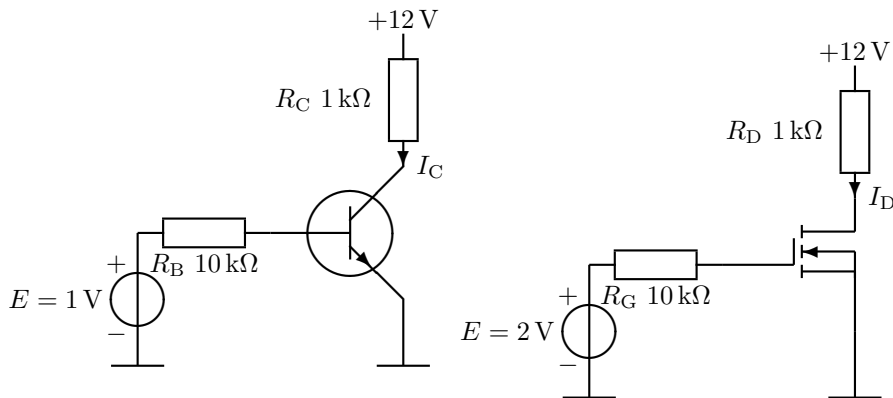a) Draw a circuit diagram for a circuit which fulfills the function  $U_{out} = 2U_{in}$  (3 points).



- b) Find the current  $I_C$  (3 points). The current gain of the transistor is  $\beta = 100$ .  
 c) Find the current  $I_D$ . For the MOSFET:  $U_T = 3 \text{ V}$  and  $K = 50 \frac{\text{mA}}{\text{V}^2}$  (3 points).  
 d) If the collector resistor  $R_C$  were  $100 \text{ k}\Omega$ , how large is  $I_C$ ? (1 point)

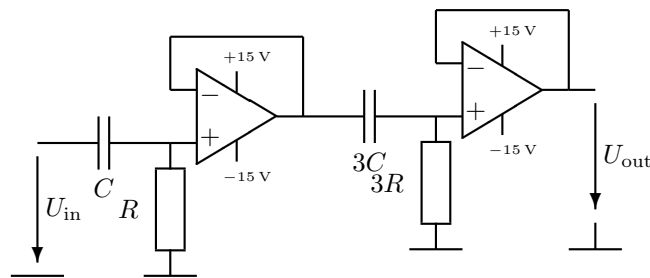

**Assignment 4**

- a) Is the circuit a low-pass or a high-pass filter (1 points)? Calculate the transfer function for the circuit (3 points), find the characteristic frequency  $f_0$  (2 points) and the damping coefficient  $D$  (2 points).  
 b) A transfer function for a Bessel filter is

$$F(s) = \frac{3}{s^2 + 3s + 3}.$$

Using this function, design a 2nd order Bessel low-pass filter, for which the half-power frequency is at  $\omega = 10$ . Calculate the characteristic angular frequency  $\omega_0$  (1 point) and the damping coefficient  $D$  for the filter (1 point).

Bonus question (2 points): Draw the circuit diagram (with component values) for the filter you designed.