

**S-87.2113 Basic electronics Exam 27.09.2009 / Marko Kosunen**

Write your name and your student number on every paper (also on possible appendices). All calculators allowed. NO literature allowed.

1. a) Derive an expression for the voltage gain  $v_o/v_{in}$  of the operational amplifier circuit in Fig. 1.
  - b) Design the circuit so that its voltage gain is 26dB and its input impedance is  $10k\Omega$ .
  - c) The operational amplifier has an input offset voltage  $V_{OF} = 10mV$ . Calculate the error voltage at the amplifier output.
  - d) The amplifier is changed so that a capacitor  $C$  is connected in series with  $R_1$ . How large are the error voltages due to offset voltage and bias current now?
- Hint: the sign of  $V_{OF}$  is not important.

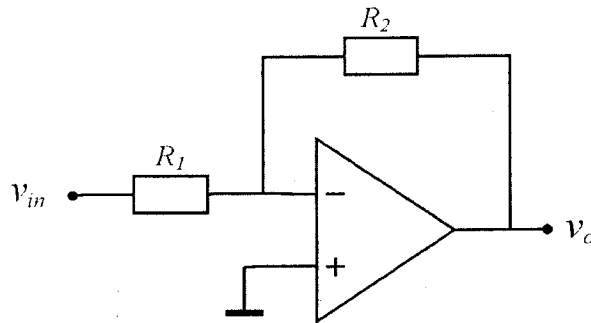


Figure 1:

- 2 a) Design the circuit of the figure 2 so that the voltage gain is 10 and the current through the feedback resistor is at most 1mA when the output voltage is 1V. Assume that the operational amplifier is ideal.
- b) If the gain of the operational amplifier is not infinite but 80dB, how large is the error due to finite gain in the circuit of a)-part? How large is the error if the overall gain of the circuit should be 200.

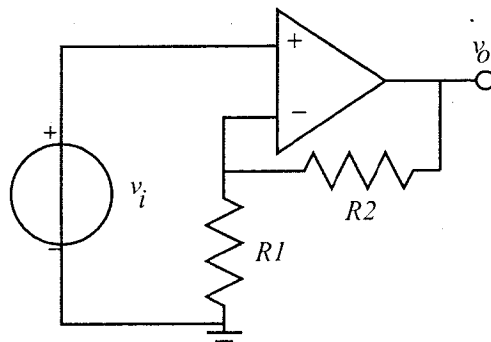


Figure 2:

3. The component values in the amplifier of Fig.3 are as follows:  $R_1 = 6k\Omega$ ,  $R_2 = 1k\Omega$ ,  $R_3 = 10k\Omega$ ,  $k'_n \frac{W}{L} = 4mA/V^2$ ,  $V_t = 1V$  and  $V_{DD} = 10V$ ,  $i_d = k'_n \frac{W}{2L} (v_{GS} - V_T)^2 (1 + \lambda v_{DS})$ . You can neglect the channel length modulation of the MOS transistor. Further, the capacitors are big with respect to the frequency of interest.

- Find the operating point of the transistor.
- Draw the small signal equivalent circuit of the amplifier.
- Determine the open circuit voltage gain  $A_{vo}$  and the input and output impedances  $R_{in}$  and  $R_o$ .
- How much  $R_1$  and  $R_2$  lower the output voltage when the internal source impedance is  $1k\Omega$ ?

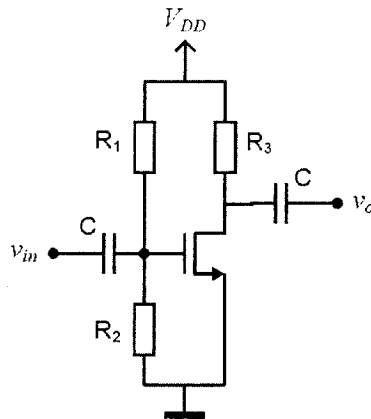


Figure 3:

- Draw the output voltage of the circuit in Fig. 4 in continuous state (not the start-up transient), when the input voltage is  $v_i(t) = 1 + 3 \cdot \sin(2\pi 1kHz \cdot t)V$  and the load resistor  $R_L$  is infinite. Assume that the diode is ideal (no resistance, no forward voltage drop).
  - Draw the output voltage in continuous state when  $v_i(t) = 1 + 3 \cdot \sin(2\pi 1kHz \cdot t)V$ ,  $R_L = 100k\Omega$ ,  $C_1 = 1\mu F$  and the forward diode voltage is  $V_D = 0.7V$ . Take the droop at the output into account. (Still neglect the diode's dynamic resistance).

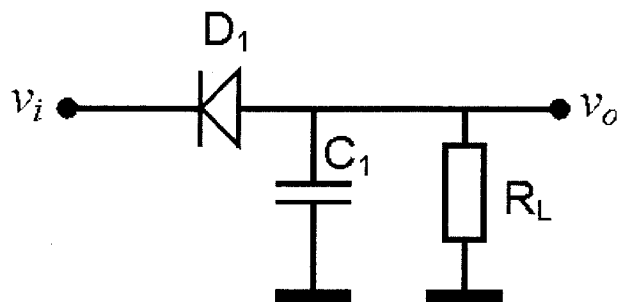


Figure 4: