

1. Explain briefly:
- small-signal analysis,
 - state-space equation,
 - Runge-Kutta method,
 - voltage behind the transient reactance and
 - operator inductance.

2. a) List the four simplifications usually made in space-vector modelling of rotating electrical machines.
- b) Verify that the instantaneous power of a three-phase system can be expressed in terms of space vectors as $p = 3/2 \operatorname{Re}\{\underline{u}^* \underline{i}\}$.

3. A one-phase transformer is connected to a sinusoidal voltage source $u = \hat{u} \cos \omega t$. Derive the differential equations of the primary and secondary currents. Solve the equations assuming that the load of the transformer is zero and the connection is done at time $t = 0$. The resistance and inductance of the primary winding are R_1 and L_1 , and those of the secondary winding R_2 and L_2 . The mutual inductance of the windings is L_m .

4. As a starting point, you have the general space-vector equations of an induction motor presented in the stator frame of reference. Derive the steady-state phasor equations of the induction motor and its one-phase, steady-state equivalent circuit.

5. After a three-phase short circuit at the terminals of a synchronous machine, the stator current in phase a and field winding current are

$$i_{sa} = -\hat{u}_{s0} \left\{ \left[\frac{1}{X_d} + \left(\frac{1}{X_d'} - \frac{1}{X_d} \right) e^{-t/T_d'} + \left(\frac{1}{X_d''} - \frac{1}{X_d'} \right) e^{-t/T_d''} \right] \cos(\omega t + \vartheta_{r0}) - \frac{1}{2} \left(\frac{1}{X_d''} + \frac{1}{X_q''} \right) e^{-t/T_a} \cos \vartheta_{r0} - \frac{1}{2} \left(\frac{1}{X_d''} - \frac{1}{X_q''} \right) e^{-t/T_a} \cos(2\omega t + \vartheta_{r0}) \right\}$$

$$i_f = i_{f0} \left[1 + \left(\frac{X_d}{X_d'} - 1 \right) e^{-t/T_d'} - \left(\frac{X_d}{X_d'} - 1 \right) e^{-t/T_a} \cos \omega t \right]$$

- To which windings are the current components and time constants associated with?
- What can you say about the relative magnitude of the time constants?
- How do the currents change if we neglect the resistances?